

Fundamentals of Electrical Engineering (EEL 101)

Minor Test #1

Time: 1 hour

Max marks 20

1. Consider the circuit shown in Fig. 1. Determine the voltage V_0 , using Thevenin's Theorem. (5)

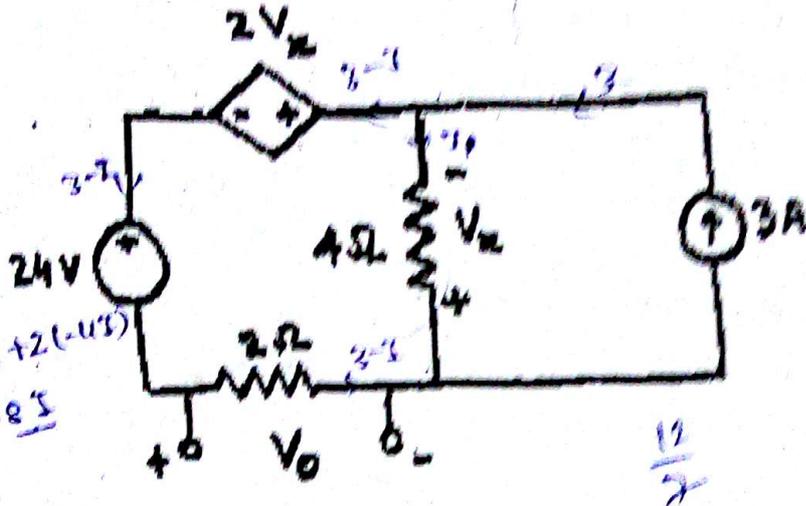


Fig. 1

$$V_x = -4I$$

$$-4I + (3-3)2 + 24 + 2(-4I)$$

$$-4I + 6 - 2I + 24 - 8I$$

$$14I = 30$$

$$I = \frac{30}{14}$$


2. In the circuit of Fig. 2, $L=2$ H, $R_1=10$ Ω , $R_2=8$ Ω and $C=(1/8)$ F. The initial conditions are given by $v_c(0) = 1$ V and $i_L(0) = (1/2)$ A.

- (a) Obtain the "homogeneous" differential equation governing the system, in terms of $v(t)$, and the "characteristic" equation.
- (b) Will the response be under, over or critically damped?
- (c) Solve for $v(t)$ and evaluate all constants from initial conditions, and plot it approximately. (6)


$$3 - \frac{30}{14}$$

$$\frac{42-30}{14} + x$$

$$e^{-3t} + 6e^{-3t}$$

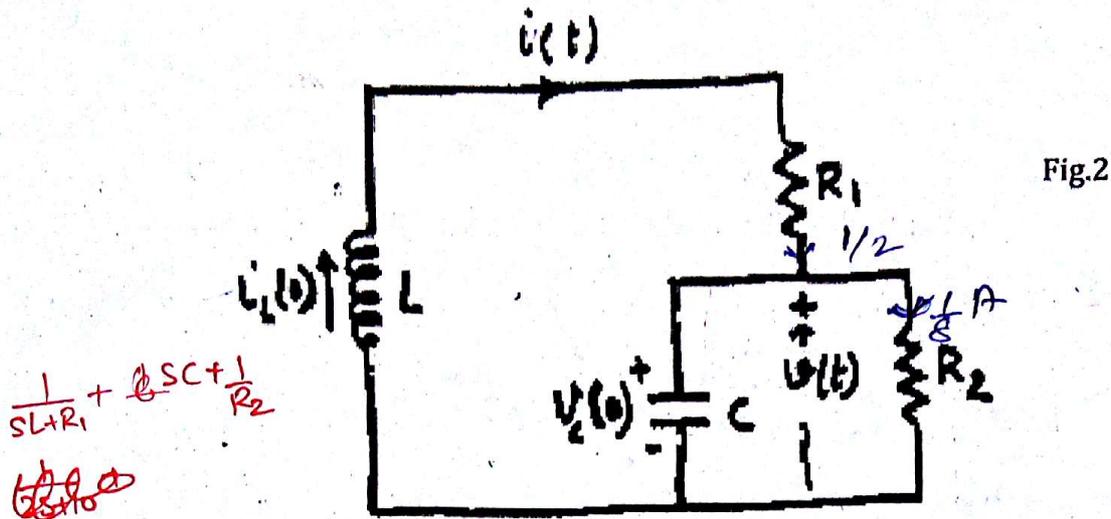

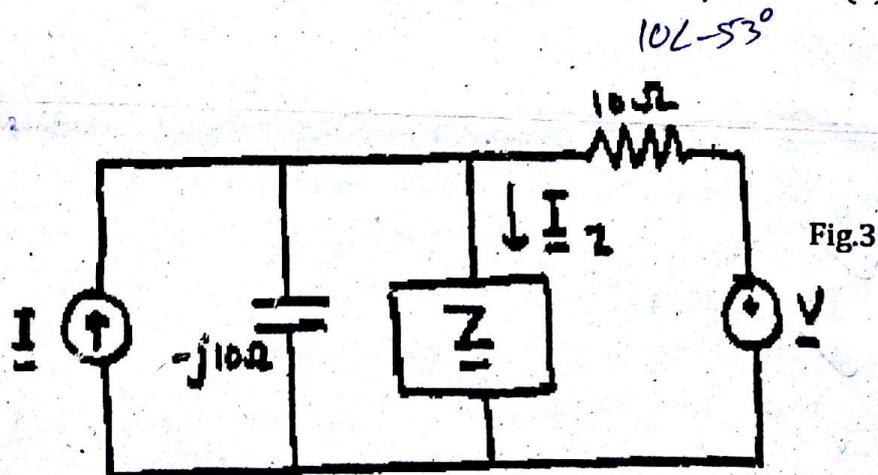3. In the Circuit of Fig. 3, we have $\underline{I} = 8\angle 0^\circ \text{ A}$, $\underline{V} = 60\angle 90^\circ \text{ V}$, $\underline{Z} = 10\angle 90^\circ \Omega$. Replace \underline{V} and the $10\text{-}\Omega$ resistance by a Norton Equivalent and predict \underline{I}_2 . Write the expression for this current as a function of time, given that both the sources generate signals at a frequency of 1000 radians/sec. (5)



4. Obtain the generic form of the natural response $v(t)$ of the system of Fig. 2 by using the pole-zero plot of an appropriately identified impedance or admittance function. Do not evaluate the constants (coefficients of the exponentials) here. (4)