

Prob.1 (a) Derive the expressions for the elements of Y-network in terms of  $\Delta$ -network and vice-versa.  
 (b) Compute the equivalent impedance, current I and current  $I_R$  for the circuit given (Fig.1)

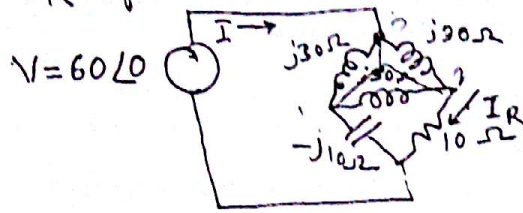


Fig.1

(5)

Prob.2 Switch S is closed at  $t=0$ . Determine the initial and final values of  $i$ ,  $V_c$ ,  $\frac{di}{dt}$  and  $\frac{dV_c}{dt}$ . Also find  $i(t)$ . (Fig.2)

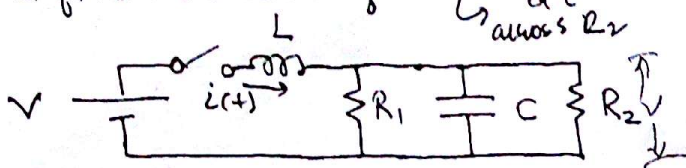


Fig.2

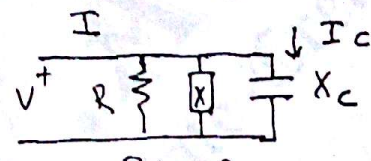


Fig.3

(5)

Prob.3 A current  $i_c = 6\sqrt{2} \cos 1000t$  Amp. flows in  $250\mu F$  capacitor (Fig.3). (i) Find  $V_c$ ; (ii) show  $V_c$  and  $I$  on phasor diagram and specify R and X. ( $I = 10 \angle -37^\circ$ )

Prob.4 Using a  $50\mu A$  movement with a  $10,000\Omega$  internal resistance (a) Design a multirange d.c. ammeter with range of  $1mA$ ,  $10mA$  and  $100mA$  (b) Design a multistage voltmeter with ranges of  $3V$ ,  $10V$ ,  $50V$  and  $150V$ .

Prob.5 The total core loss (hysteresis & eddy current) for a magnetic sheet steel is found to be  $1800$  watts at  $60$  Hz. If the flux density is kept constant and the frequency of the supply increased by  $50\%$ , the total core loss is found to be  $3000$  watts. Compute the separate hysteresis and eddy current losses in both frequencies

P.T.O.

$22 = \frac{22 \times 22}{22}$   
 $22 = \frac{22 \times 22}{22}$   
 $22 = \frac{22 \times 22}{22}$   
 $22 = \frac{22 \times 22}{22}$

(5)

(1)