

**Fundamentals of Electrical Engineering (EEL 101)**  
**Major Test**

Time: 2 Hours.

Max. Marks 30

1. (a) A balanced  $\Delta$ -connected load contains a  $10 \Omega$  resistor in series with a  $20 \text{ mH}$  inductor in each phase. The voltage source is an  $abc$ -sequence three-phase  $60 \text{ Hz}$  balanced wye with a voltage  $V_{an} = 120 \angle 30^\circ \text{ rms}$ . Determine all  $\Delta$ -currents and line currents.  $16.6 \angle -37^\circ, 28.75 \angle -7^\circ$  (3)  $1\frac{1}{2}$
- (b) A three-phase balanced  $Y$ - $\Delta$  system has a line voltage of  $208 \text{ V rms}$ . The total real power absorbed by the load is  $1200 \text{ W}$ . If the power factor of the load is  $20^\circ$  lagging, determine the value of the line current and the value of the load impedance per phase in the delta.  $58.75 \angle 20^\circ$  (3) 3

2. A  $12 \text{ kW}$  shunt-connected dc generator is rated at  $240 \text{ V}$ ,  $50 \text{ A}$ , and  $1000 \text{ rpm}$ . Under no-load conditions, the generated voltage is  $255 \text{ V}$ . For full load conditions, neglect the field current compared with the armature current and calculate the armature resistance. 0.3 (3) 3

3. Show that when the secondary of a transformer is connected to an impedance  $Z_L$ , an equivalent model can be obtained as shown in Fig. P3 by referring all quantities to the primary side. Also find the values of  $R_{E1}$  and  $X_{E1}$  in this model, (3)

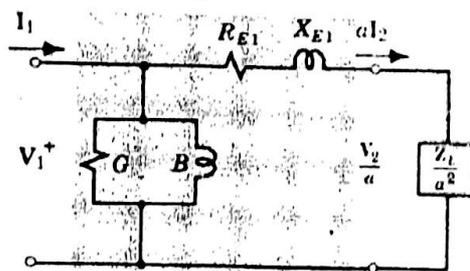


Fig. P3

4. The core of Fig. P4 is Armco iron with  $a = c = 15 \text{ cm}$  and  $b = d = 35 \text{ cm}$ ; the current in the  $350$ -turn coil is  $15 \text{ A}$ . Estimate the allowable air-gap length for a magnetic flux of  $12 \text{ mWb}$ . Also estimate the error in percent that result from neglecting the mmf drop in the iron. Assume that a flux density of  $B = 0.53 \text{ T}$  requires a field intensity  $H = 80 \text{ At/m}$ . (4) 4

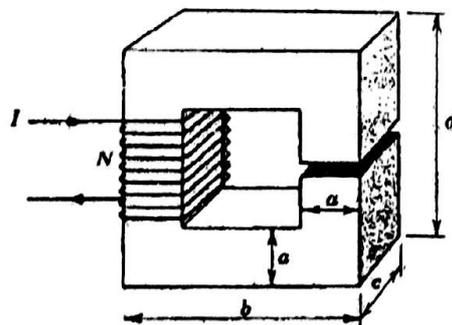


Fig. P4

5. The circuit of Fig. P5 is called a General Impedance Converter. Develop an expression for the equivalent impedance  $Z_{eq} (= V_{in}/I_{in})$  in terms of  $Z_1, Z_2, Z_3, Z_4$  and  $Z_5$ . Based on the resulting expression, use resistors of equal

$$a^2 \frac{1}{Z_2} R_{E1} = \frac{1}{Z_2} R^2$$

$$R_{E1} = R$$

5

value and a 1- $\mu\text{F}$  capacitor, to realize an inductance of 1 H. Can you see a purpose to go to all this trouble for realizing an inductor? Explain briefly. Hint: Assuming ideal op-amps, voltages at nodes E, C and A are each equal to  $V_{in}$ . (6)


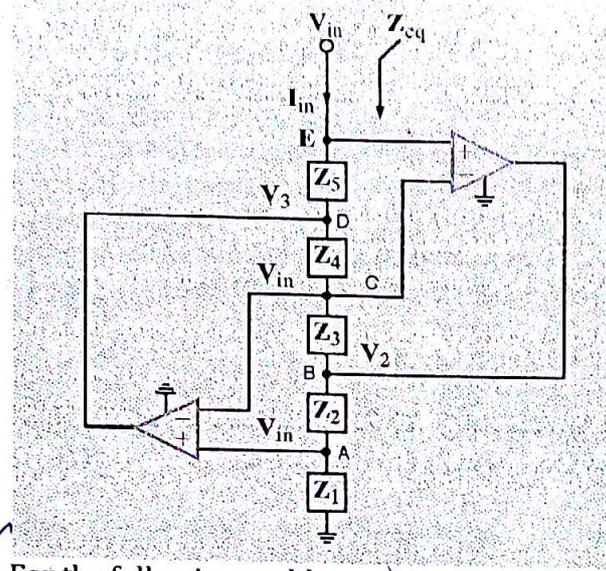


Fig. P5


6. For the following problems, do your calculations as required on a rough page. Only indicate the correct solution by writing the correct choice together with the answer. Thus, the answer should be written in the form: (i) 10A, etc., as applicable in each case. Clearly designate one of the pages of your answer sheet for rough work for Question 6 to check that the answers have been calculated by you. (8)

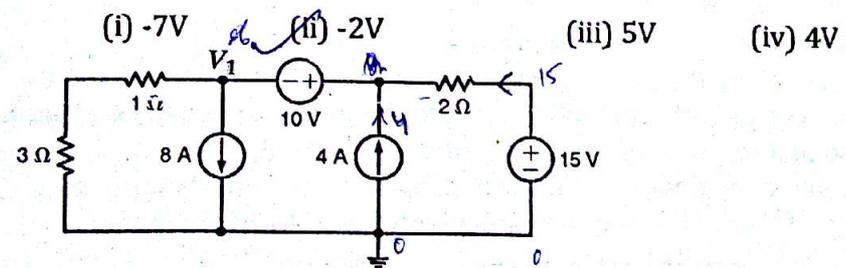(a) What is the value of the voltage  $V_1$  in the circuit shown below.




(b) In the network shown below, the switch closes at  $t = 0$ . Find  $v_o(t)$  at  $t = 1\text{s}$ .

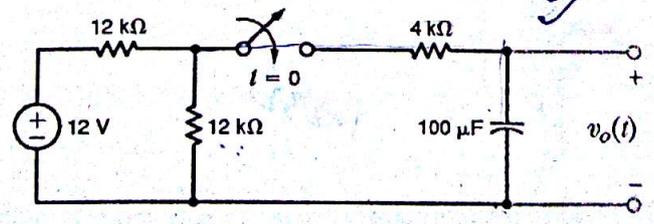- (i) 5.62 V    (ii) 1.57 V    (iii) 4.25 V    (iv) 3.79 V



(c) Given the low-pass filter circuit shown below, find the frequency in Hz at which the output is down 3dB from the dc or very low-frequency output.

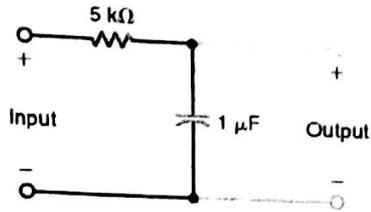- (i) 26 Hz     (ii) 60 Hz    (iii) 47 Hz    (iv) 32 Hz.



(d) A two-port network is known to have the following parameters:  $y_{11} = \frac{1}{14} S$ ;  $y_{12} = y_{21} = -\frac{1}{21} S$ ;  $y_{22} = \frac{1}{7} S$ . If a 2A current source is applied at the input terminals as shown in the figure below, find the voltage across the current source.

- (i) 36V    (ii) 12V    (iii) 24V    (iv) 6V

